Bomere and the XI Towns Federation Knowledge Organiser—Science

Topic:- Science—Electricity

Class/Year Groups: Year 4

Term: Autumn

What you already know?

This is the first time that pupils will have studied electricity in detail.

Materials can be tested in a circuit to see if they are electrical conductors or electrical insulators.







10p = metal = electrical conductors test circuit


bulb: Lights up in a

complete circuit.

ruler = plastic = electrical insulators


buzzer: Makes a noise in

a complete circuit.

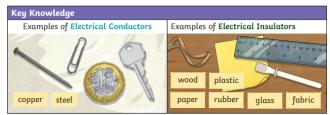


To work safely with circuit components in the classroom:

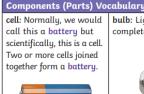- None of the equipment needs to use mains power, so do not put any of it in or near plugs.
- Report any damaged or broken equipment to uour teacher. Do not use it.
- · Only use equipment as instructed.
- Connect equipment correctly.
- Disconnect equipment after use and put it away neatly.





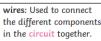











switch: Used to turn



Electricity	The flow of an electric current
	through a material, e.g. from a power
	source through wires to an appliance.

Circuit A pathway that electricity can flow

around. It is based around wires and a power supply. Examples of components (parts) you can add in to a circuit are bulbs, switches, buzzers and

motors.

Battery A device that stores electrical energy

> as a chemical. Two or more cells joined together form a battery.

A piece of equipment or a device **Appliances**

> designed to perform a particular job, such as a washing machine or mobile

phone.

Electrical Conductor

A conductor of electricity is a material that will allow electricity to flow

through it.



National Curriculum Objectives:

- Identify common appliances that run on electricity.
- Construct a simple series electrical circuit, identifying and naming its basic parts, including cells, wires, bulbs, switches and buzzers.
- Identify whether or not a lamp will light in a simple series circuit, based on whether or not the lamp is part of a complete loop with a battery.
- Recognise that a switch opens and closes a circuit and associate this with whether or not a lamp lights in a simple series circuit.
- Recognise some common conductors and insulators, and associate metals with being good conductors.

